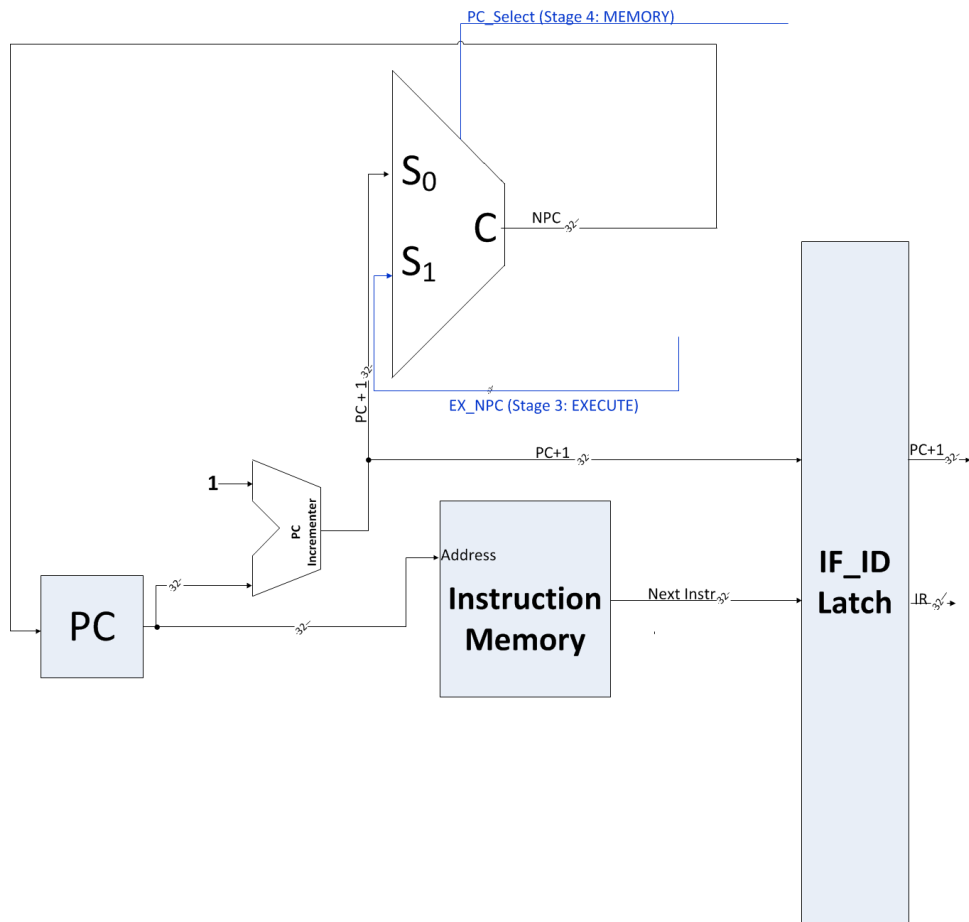


# 1 Instruction Fetch

The first stage of the MIPS processor is the instruction fetch stage (IF). This is the stage where the instructions are fetched from memory. The objective of this lab is to fully implement and understand the first stage of the MIPS processor data path.



## 1.1 Components

List of Stage 1 Components

 


Figure 1: The PC register holds the current value of the Program Counter (PC). It takes in as its input a 32-bit number which represents the New Program Counter (NPC), updates the current PC to the NPC value, and outputs the results to all dependent modules. See **listing 1** for corresponding Verilog code block.

 


Figure 2: The Incrementer takes in the current PC value and outputs the next PC value. It takes in as its input a 32-bit constant 1 and the 32-bit PC. It adds the two inputs together and outputs the result. See **listing 2** for corresponding Verilog code block.

 


Figure 3: The MUX takes in the next sequential PC value, the PC value calculated in Stage Three: Execute, and outputs value specified via the select line from Stage Four: Memory. When the select line from the MEM stage is low (0), it will output the next sequential PC Value. When the line goes high (1) it will output the value calculated in the Execute stage. See **listing 3** for corresponding Verilog code block.

 


Figure 4: The Instruction Memory module takes in the current 32-bit PC value as its input and outputs the 32-bit instruction which that PC value is currently pointing at. See **listing 4** for corresponding Verilog code block.

## 1.2 Code

Listing 1: Code for the Program Counter Module

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Program Counter Module
/////////////////////////////////////////////////////////////////
module pc(input [31:0] npc,
          output reg [31:0] pc_out
);

    initial
    begin
        /* Initial Thread which will set pc_out to zero on
           the first run
        */
        pc_out <= 0;
    end

    always @ (npc)
    begin
        #1
        /* update value of PC to New Program Counter */
    end

endmodule

```

 


Figure 5: The Instruction Fetch-Decode latch (IF\_ID\_Latch). This latch takes in the next sequential PC value and address and outputs them to the next stage. See **listing 5** for corresponding Verilog code block.

Listing 2: Code for the Incrementer Module

```
'timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Incrementer Module which accepts the Program Counter
// and adds 1 to it.
/////////////////////////////////////////////////////////////////
module incrementer(
```

```

        input wire [31:0] pc_in ,
        output wire [31:0] pc_out

    );

assign pc_out = /* add 1 to pc_in */;
endmodule

```

Listing 3: Code for the MUX Module

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
//
//  Multiplexor Module which will pick between
//  the next sequential PC value and
//  the PC Value calculated in the Execute stage
//  depending on the value of the select line
//  set in the Memory stage.
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module mux(input [31:0] s0 , s1 ,
          input select ,
          output [31:0] npc
        );

assign npc = /* if select is high
              then npc = s1.

              If select is low
              then npc = s0.

              Use a ternary operator
              to write this statement
              */;

endmodule

```

Listing 4: Code for the Instruction Memory Module

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Memory module which holds all of the instructions
// needed by the MIPS processor
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module mem(
    input [31:0] addr ,
    output reg [31:0] data

```

```

    );

    reg [31:0] MEM[0:127];

    initial
    begin
        MEM[0] <= 'hA00000AA;
        MEM[1] <= 'h10000011;
        MEM[2] <= 'h20000022;
        MEM[3] <= 'h30000033;
        MEM[4] <= 'h40000044;
        MEM[5] <= 'h50000055;
        MEM[6] <= 'h60000066;
        MEM[7] <= 'h70000077;
        MEM[8] <= 'h80000088;
        MEM[9] <= 'h90000099;
    end

    always @(addr)

    begin
        data <= MEM[ addr ];
    end

endmodule

```

Listing 5: Code for the IF\_ID Latch

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Latch witch passes data from the Fetch Stage to
// the Decode Stage.
/////////////////////////////////////////////////////////////////
module IF_ID(
    input wire [31:0] instruction_in , npc_in ,
    output reg [31:0] instruction_out , npc_out
);

    initial
    begin
        instruction_out <= 0;
        npc_out <= 0;
    end

    always @ *
    begin

```

```

        #1
        /* update instruction_out and npc_out values
           with new instruction and npc values from
           the Fetch stage.
        */

end
endmodule

```

Listing 6: Code for the top level Instruction Fetch Module

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// The top level module for the Instruction Fetch Stage.
// This is how all of the individual modules are
// connected to each other.
/////////////////////////////////////////////////////////////////
module IFETCH(
    input EX_MEM_PCSrc,
    input wire [31:0] EX_MEM_NPC,
    output wire [31:0] IF_ID_INSTR, IF_ID_NPC
);

//signals
    wire [31:0] PC;
    wire [31:0] dataout;
    wire [31:0] npc, npc_mux;

//instantiations
    mux mux_1 (.npc(npc_mux),
               .s1(EX_MEM_NPC),
               .s0(npc),
               .select(EX_MEM_PCSrc));

    pc pc_1 (.pc_out(PC),
             .npc(npc_mux));

    mem mem_1 (.data(dataout),
               .addr(PC));

    IF_ID IF_ID_1 (.instruction_out(IF_ID_instr),
                  .npc_out(IF_ID_npc),
                  .instruction_in(dataout),
                  .npc_in(npc));

```



```

    incremter incrementer1 (.pc_out(npc),
                           .pc_in(PC));

endmodule

```

### 1.3 Testbenches & Timing Diagrams

Listing 7: Instruction Fetch Test Bench

```

`timescale 1ns / 1ps

////////////////////////////////////
//  Stage 1 Test Bench
////////////////////////////////////

module IFETCH_TEST;

    // Inputs
    reg EX_MEM_PCSrc;
    reg [31:0] EX_MEM_NPC;

    // Outputs
    wire [31:0] IF_ID_INSTR;
    wire [31:0] IF_ID_NPC;

    // Instantiate the Unit Under Test (UUT)
    IFETCH uut (
        .EX_MEM_PCSrc(EX_MEM_PCSrc),
        .EX_MEM_NPC(EX_MEM_NPC),
        .IF_ID_INSTR(IF_ID_INSTR),
        .IF_ID_NPC(IF_ID_NPC)
    );

    initial
    begin
        EX_MEM_NPC = 0;
        EX_MEM_PCSrc = 0;
        #9
        EX_MEM_PCSrc = 1;
        EX_MEM_NPC = 5;
        #1
        EX_MEM_PCSrc = 0;
        #10;
        $stop;
    end

```


```

end

endmodule

```

Figure 6: Instruction Fetch Stage Simulation.

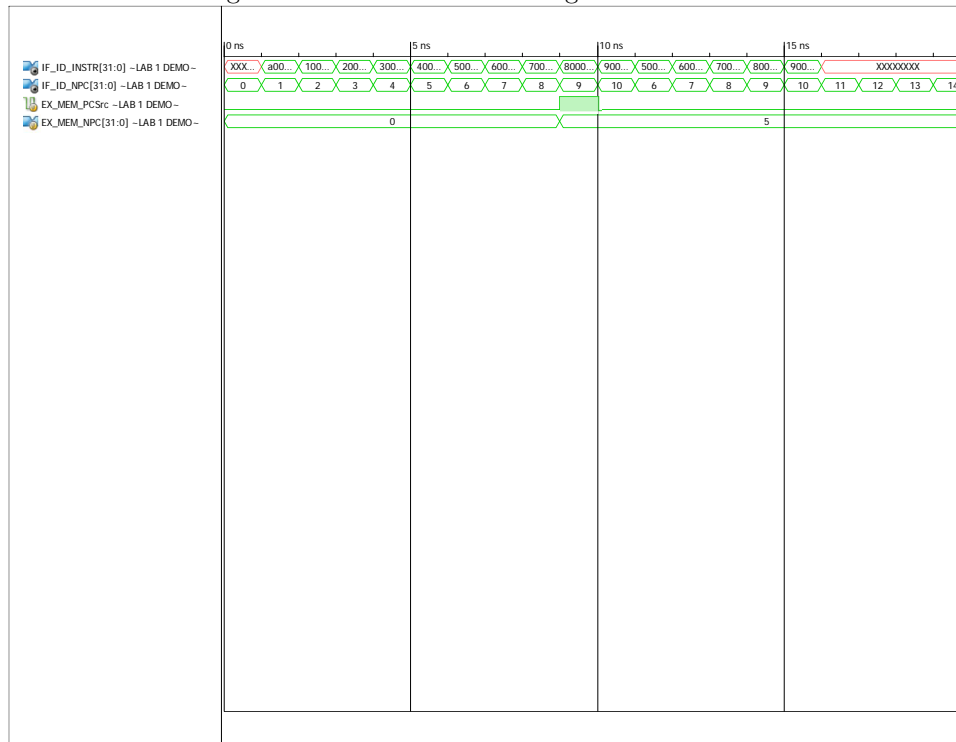

## 1.4 What to turn in

Fully implement all of the components listed in **section 1.1**. You may use the code provided in **section 1.2**. Run a full *20 ns* simulation and demonstrate successful instruction fetch routines. For this test show your Program Counter incrementing sequentially for the *first 10 ns* then emulate out of order PC jumps. Compare your results to **Figure 6**. Turn in a lab report as outlined by your lab instructor and be ready to demonstrate your code if asked.